



ELEX 7660: Digital System Design

Lab 4

Student Name: Taewoo Kim	Student Number: A01284763	Set: T
--------------------------	---------------------------	--------

Table of Contents


1	Screenshot of the simulations.....	3
2	Source code of the module	4
2.1	Lab4.sv code	4
2.2	adcinterface.sv code	5
2.3	enc2chan.sv	8
3	Quartus compilation report	10
4	RTL Netlist.....	11
4.1	Overall view (lab4 module).....	11
4.2	enc2chan.sv	11
4.3	adcinterface.sv.....	11

1 Screenshot of the simulations



```
add wave sim:/adcinterface_tb/*
```

```
VSIM 3> run -all
```

```
# ADC output check - PASS: expected ADC ouput 3b8, received 3b8
# Config word Check - PASS: channel 0, expected config word 22, received 22
# ADC output check - PASS: expected ADC ouput c26, received c26
# Config word Check - PASS: channel 1, expected config word 32, received 32
# ADC output check - PASS: expected ADC ouput 966, received 966
# Config word Check - PASS: channel 2, expected config word 26, received 26
# ADC output check - PASS: expected ADC ouput 3b6, received 3b6
# Config word Check - PASS: channel 3, expected config word 36, received 36
# ADC output check - PASS: expected ADC ouput 8c6, received 8c6
# Config word Check - PASS: channel 4, expected config word 2a, received 2a
# ADC output check - PASS: expected ADC ouput e46, received e46
# Config word Check - PASS: channel 5, expected config word 3a, received 3a
# ADC output check - PASS: expected ADC ouput f72, received f72
# Config word Check - PASS: channel 6, expected config word 2e, received 2e
# ADC output check - PASS: expected ADC ouput 32e, received 32e
# Config word Check - PASS: channel 7, expected config word 3e, received 3e
# ** Note: $stop : C:/Users/Taewoo Kim/Desktop/Test/adcinterface_tb.sv(63)
# Time: 289 ms Iteration: 1 Instance: /adcinterface_tb
# Break in Module adcinterface_tb at C:/Users/Taewoo Kim/Desktop/Test/adcinterface_tb.sv line 63
```

 

Zoomed in pictures:

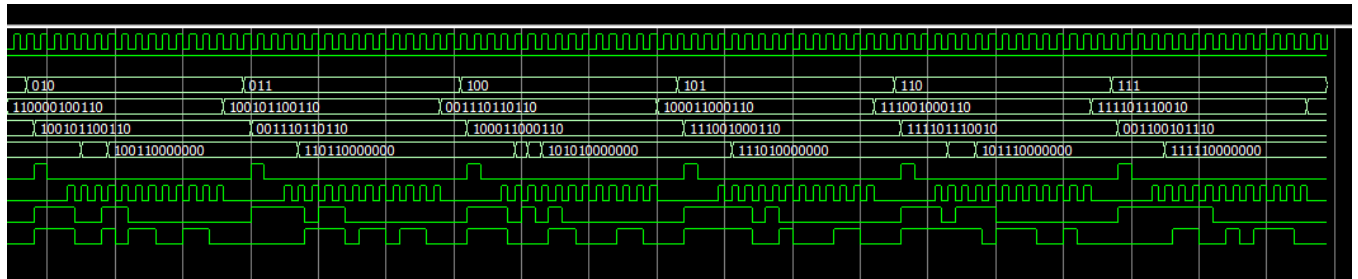 

2 Source code of the module

2.1 Lab4.sv code

```
// File: lab4.sv
// Description: ELEX 7660 lab4 top-level module.
//           We can use enc to select analog channel
//           and use adc to convert analog to digital bits and display on
//           7-segments
// Author: Taewoo Kim
// Date: 2025-02-10

module lab4 (
    input logic CLOCK_50,           // 50 MHz clock input
    (* altera_attribute = "-name WEAK_PULL_UP_RESISTOR ON" *)
    input logic enc1_a, enc1_b,     // Encoder 1 signals (A and B channels)
    input logic s1,                 // Pushbuttons for reset (s1) and turning On/Off
    input logic ADC_SDO,
    output logic [7:0] leds,        // 7-segment LED display output
    output logic ADC_CONVST, ADC_SCK, ADC_SDI,
    output logic [3:0] ct           // Digit cathodes for the 7-segment display
);

    logic [1:0] digit; // select digit to display
    logic [3:0] disp_digit; // current digit of count to display
    logic [15:0] clk_div_count; // count used to divide clock
    logic enc1_cw, enc1_ccw; // enc1 cw/ccw variables
    logic [11:0] adc_values; // variable to store adc vals
    logic [2:0] channel_values; // variable to store channel vals

    // instantiate modules to implement design
    decode2 decode2_0 (.digit, .ct);
    // instantiate decode 7 to display digit on leds
    decode7 decode7_0 (.num(disp_digit), .leds);

    // instantiate encoders
    encoder encoder_1
    (.clk(digit), .a(enc1_a), .b(enc1_b), .cw(enc1_cw), .ccw(enc1_ccw));

    // instantiate encoder to channel
    enc2chan enc2chan_1
    (.clk(clk_div_count[13]), .reset_n(s1), .cw(enc1_cw), .ccw(enc1_ccw), .chan(channel_v
alues));

    // instantiate adc interface module
    adcinterface adcinterface_1
    (.clk(clk_div_count[13]), .reset_n(s1), .chan(channel_values), .result(adc_values), .
ADC_SDO, .ADC_CONVST, .ADC_SCK, .ADC_SDI);
```

```

    // use count to divide clock and generate a 2 bit digit counter to determine which
    digit to display
    always_ff @(posedge CLOCK_50)
        clk_div_count <= clk_div_count + 1'b1 ;

    // assign the top two bits of count to select digit to display
    assign digit = clk_div_count[15:14];

    // Select digit to display (disp_digit)
    // Left two digits (3,2) display encoder 1 hex count and right two digits (1,0)
    display encoder 2 hex count
    always_comb begin
        // according to enc1_counts or enc2_counts value set disp_digit accordingly to
        set the leds
        case (digit)
            2'b00: disp_digit = adc_values[3:0];    // display adc values digit 0
            2'b01: disp_digit = adc_values[7:4];    // display adc values digit 1
            2'b10: disp_digit = adc_values[11:8];   // display adc values digit 2
            2'b11: disp_digit = {1'b0, channel_values}; // display # of analog channel
            default: disp_digit = 4'd0;
        endcase
    end
endmodule

```

2.2 adcinterface.sv code

```

// File: adcinterface.sv
// Description: adcinterface module to integrate ltc2308 adc
// Author: Taewoo Kim
// Date: 2025-02-10

module adcinterface(
    input logic clk, reset_n,    // clock and reset signals: 'clk'
    for timing, 'reset_n' active low reset.
    input logic [2:0] chan,      // ADC channel to sample, 3 bits
    wide to select channel and configuration bits.
    output logic [11:0] result, // 12-bit ADC result output from
    the ADC conversion.

    // ltc2308 signals
    output logic ADC_CONVST, ADC_SCK, ADC_SDI,
    input logic ADC_SDO
);

```

```

// patterns:
//
// ADC_CONVST   Output   Conversion Start - Triggers ADC conversion.
// ADC_SCK      Output   Serial Clock - Clocks data in/out (like SPI).
// ADC_SDI      Output   Serial Data Input - Sends config commands to ADC.
// ADC_SDO      Input    Serial Data Output - Receives 12-bit ADC result.

/*
    adc_counter  ADC_CONVST  ADC_SCK      Event
    0            1          0            Start ADC conversion (Pulse CONVST).
    1            0          0            Hold CONVST low for 1 cycle.
    2-13         0          clk          Toggle SCK for 12 cycles (data transfer).
    14-15        0          0            Wait before restart.
*/

logic [3:0] adc_counter; // 4-bit counter to keep track of the ADC state
sequence.
logic [5:0] SDI_init;    // 6-bit register used to hold and shift out
configuration bits to the ADC.
logic [11:0] SDO_temp;   // Temporary 12-bit register to hold serial data
received from ADC before finalizing.

// Combinational block: defines outputs ADC_SDI, ADC_CONVST, and ADC_SCK based on
adc_counter and clock.
always_comb begin
    ADC_SDI = SDI_init[5]; // Drive ADC_SDI with the most significant bit of
the configuration register.
    ADC_CONVST = (adc_counter == 4'd0) ? 1'b1 : 1'b0; // Generate a high pulse
on ADC_CONVST when adc_counter is 0, triggering a conversion.
    // For ADC_SCK, during states 2 to 13, output the system clock to drive
ADC_SCK; otherwise, hold it low.
    ADC_SCK = (adc_counter >= 2 && adc_counter <= 13) ? clk : 1'b0;
end

// Sequential block: Negative edge of clock or negative reset, updating the
adc_counter.
always_ff @(negedge clk, negedge reset_n) begin
    if(~reset_n) begin
        adc_counter <= 4'd0; // On reset (active low), initialize adc_counter to
0.
    end else adc_counter <= adc_counter + 1'b1; // Otherwise, increment the
adc_counter by 1 on every negative edge of clk.
end

/*
S/D = SINGLE-ENDED/DIFFERENTIAL BIT
O/S = ODD/SIGN BIT
S1 = ADDRESS SELECT BIT 1

```

```

        S0 = ADDRESS SELECT BIT 0
        UNI = UNIPOLAR/BIPOLAR BIT
        SLP = SLEEP MODE BIT
    */

    // Sequential block: Sets up the configuration bits for the ADC (SDI_init) based
    on the ADC_CONVST and adc_counter.
    always_ff @(posedge ADC_CONVST, negedge ADC_SCK) begin
        if (ADC_CONVST) begin
            // On the rising edge of ADC_CONVST, load SDI_init with the configuration
            bits:
                // Bit breakdown:
                //   - Single-Ended = 1,
                //   - Odd bit is taken from chan[0],
                //   - Next two bits (S1:S0) from chan[2:1],
                //   - Unipolar = 1,
                //   - Sleep = 0.
                SDI_init <= { 1'b1, chan[0], chan[2:1], 1'b1, 1'b0 };
            end
            else if (adc_counter >= 4'd2 && adc_counter <= 4'd7) begin
                // Between adc_counter values 2 and 7, shift SDI_init left by one bit.
                // The left shift moves the current MSB out and introduces a 0 at the
                LSB.
                SDI_init <= {SDI_init[4:0], 1'b0};
            end
        end

    // Sequential block: Captures ADC_SDO data into SDO_temp on the positive edge of
    ADC_SCK or negative reset.
    always_ff @(posedge ADC_SCK, negedge reset_n) begin
        if (~reset_n) begin
            SDO_temp <= 12'b0; // On reset, clear the temporary data register.
        end
        else if (adc_counter >= 2 && adc_counter <= 13) begin
            // During the data transfer phase (adc_counter from 2 to 13), shift in
            ADC_SDO bit by bit.
            // The previous 11 bits in SDO_temp are shifted left, and the new bit is
            concatenated at LSB.
            SDO_temp <= {SDO_temp[10:0], ADC_SDO};
        end
    end

    // Sequential block: At the negative edge of ADC_SCK, finalize and store the
    conversion result.
    always_ff @(negedge ADC_SCK, negedge reset_n) begin
        if (~reset_n) begin
            result <= 12'b0; // On reset, clear the final ADC result.
        end
    end

```

```

        end
        else if (adc_counter == 13) begin
            result <= SDO_temp; // When adc_counter reaches 13, assign the captured
12-bit data to result.
        end
    end
end

endmodule

```

2.3 enc2chan.sv

```

// File: enc2chan.sv
// Description: Module using cw or ccw inputs to generate the desired channel scale
// Author: Taewoo Kim
// Date: 2025-02-10

module enc2chan (
    input logic      cw, ccw,          // Encoder signals: cw and ccw
    output logic [2:0] chan,          // Desired channel output
    input logic      reset_n, clk     // Asynchronous reset and clock
);

    // Array of channel scales (frequency levels)
    logic [2:0] chan_array [7:0] = '{3'b111, 3'b110, 3'b101, 3'b100, 3'b011, 3'b010,
3'b001, 3'b000};

    // Count threshold (pulse counter)
    localparam logic [1:0] PULSE_COUNTER = 2'b11;

    // Pulse counters for cw and ccw signals
    logic [1:0] cw_counter, ccw_counter;
    // Main channel index counter
    logic [2:0] counter;

    // Registers to store previous states for edge detection
    logic cw_prev, ccw_prev;

    // Edge detection: capture previous cw and ccw values
    always_ff @(posedge clk, negedge reset_n) begin
        // initialize cw_prev and ccw_prev
        if (!reset_n) begin
            cw_prev <= 1'b0;
            ccw_prev <= 1'b0;
            // every clock edge store cw/ccw to cw_prev/ccw_prev
        end else begin
            cw_prev <= cw;
            ccw_prev <= ccw;

```



```

        end
    end

    // Generate one-shot pulses on the rising edge of cw or ccw,
    // and ensure they are mutually exclusive
    logic cw_edge, ccw_edge;
    assign cw_edge = (cw && !cw_prev) && !ccw;
    assign ccw_edge = (ccw && !ccw_prev) && !cw;

    // Update counters on detected rising edges
    always_ff @(posedge clk, negedge reset_n) begin
        if (!reset_n) begin
            cw_counter    <= 2'b0;
            ccw_counter    <= 2'b0;
            counter        <= 3'b0;
        end else begin
            // CW handling: if a rising edge is detected on cw
            if (cw_edge) begin
                if (cw_counter == PULSE_COUNTER) begin
                    cw_counter <= 2'b0;
                    counter    <= counter + 1; // Increment channel index
                end else begin
                    cw_counter <= cw_counter + 1;
                end
            end
            // CCW handling: if a rising edge is detected on ccw
            else if (ccw_edge) begin
                if (ccw_counter == PULSE_COUNTER) begin
                    ccw_counter <= 2'b0;
                    counter    <= counter - 1; // Decrement channel index
                end else begin
                    ccw_counter <= ccw_counter + 1;
                end
            end
            // Optionally, you might reset the counters if no edge is detected:
            else begin
                cw_counter <= cw_counter;
                ccw_counter <= ccw_counter;
            end
        end
    end

    // Assign the channel output based on the channel index
    assign chan = chan_array[counter];
endmodule


```

3 Quartus compilation report


Flow Status	Successful - Sun Feb 16 22:51:53 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	lab4
Top-level Entity Name	lab4
Family	Cyclone V
Device	5CSEMA4U23C6
Timing Models	Final
Logic utilization (in ALMs)	36 / 15,880 (< 1 %)
Total registers	62
Total pins	20 / 314 (6 %)
Total virtual pins	0
Total block memory bits	0 / 2,764,800 (0 %)
Total DSP Blocks	0 / 84 (0 %)
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 5 (0 %)
Total DLLs	0 / 4 (0 %)

4 RTL Netlist

4.1 Overall view (lab4 module)

 

4.2 enc2chan.v

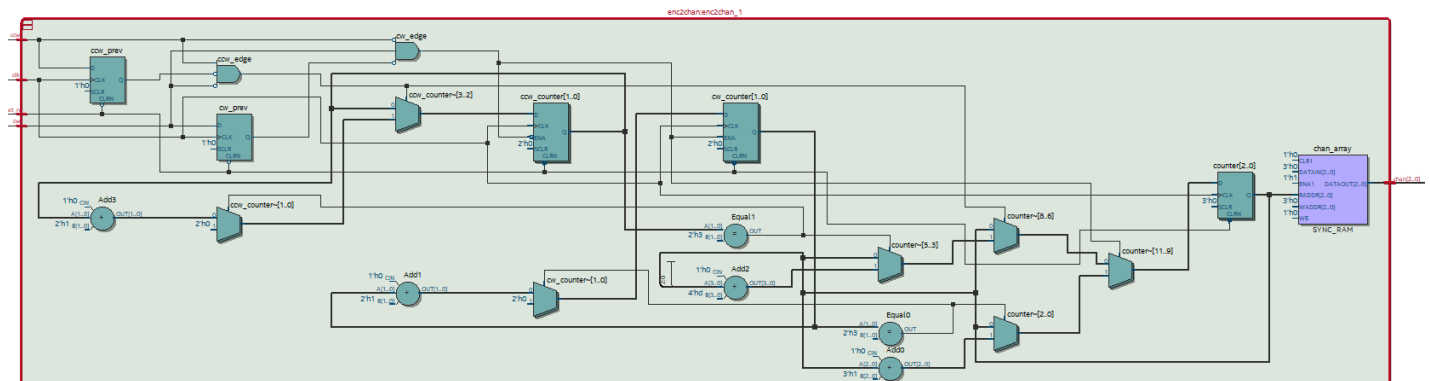

4.3 adcinterface.v

